

## **Boolean Algebra**

- Boolean algebra is used to analyze and simplify the digital (logic) circuits. It uses only the binary numbers i.e. 0 and 1. It is also called as Binary Algebra or logical Algebra.
- Boolean algebra was invented by **George Boole in 1854.**

### **Rule in Boolean Algebra**

Following are the important rules used in Boolean algebra.

- Variable used can have only two values. Binary 1 for HIGH and Binary 0 for LOW.
- Complement of a variable is represented by an overbar (-). Thus, complement of variable B is represented as  $\overline{B}$ . Thus if  $B = 0$  then  $\overline{B} = 1$  and  $B = 1$  then  $\overline{B} = 0$ .
- ORing of the variables is represented by a plus (+) sign between them. For example ORing of A, B, C is represented as  $A + B + C$ .
- Logical ANDing of the two or more variable is represented by writing a dot between them such as A.B.C. Sometime the dot may be omitted like ABC.

### **Boolean Function**

- A Boolean Function is described by an algebraic expression called Boolean expression which consists of binary variables, the constants 0 and 1, and the logic operation symbols.
- The function F is equal to 1 if x is 1 or if both y' and z are equal to 1, F is equal to 0 otherwise. Saying  $y'=1$  is equivalent to saying that  $y=0$ .
- So F is equal to 1 if  $x=1$  or if  $yz=01$ .

### **Truth Table**

- The relationship between a function in a truth table and its binary variables can be represented in a truth table.
- There are eight possible combination for assigning bits to the three variables x, y and z.

# Logic Diagrams and Expressions


Truth Table

X Y Z	$F = X + \bar{Y} \cdot Z$
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Logic Equation

$$F = X + \bar{Y} Z$$

Logic Diagram

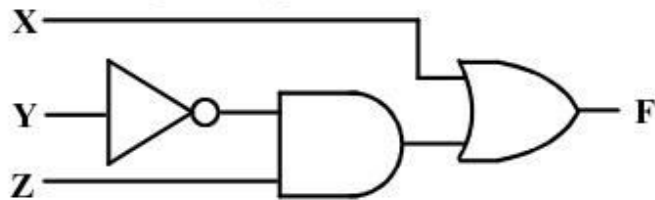

- Boolean equations, truth tables and logic diagrams describe the same function!

## Boolean Laws

There are six types of Boolean Laws.

### Commutative law

Any binary operation which satisfies the following expression is referred to as commutative operation.

$$(i) A \cdot B = B \cdot A$$

$$(ii) A + B = B + A$$

Commutative law states that changing the sequence of the variables does not have any effect on the output of a logic circuit.

### Associative law

This law states that the order in which the logic operations are performed is irrelevant as their effect is the same.

$$(i) (A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$(ii) (A + B) + C = A + (B + C)$$

## Distributive law

Distributive law states the following condition.

$$A.(B + C) = A.B + A.C$$

## AND law

These laws use the AND operation. Therefore they are called as AND laws.

$$(i) A.0 = 0$$

$$(ii) A.1 = A$$

$$(iii) A.A = A$$

$$(iv) A.\bar{A} = 0$$

## OR law

These laws use the OR operation. Therefore they are called as OR laws.

$$(i) A + 0 = A$$

$$(ii) A + 1 = 1$$

$$(iii) A + A = A$$

$$(iv) A + \bar{A} = 1$$

## INVERSION law

This law uses the NOT operation. The inversion law states that double inversion of a variable results in the original variable itself.

$$\overline{\bar{A}} = A$$

### 1. Boolean Algebra simplification rules

1. $A + \bar{A} = 1$	2. $A + A = A$
3. $A \cdot A = A$	4. $A \cdot \bar{A} = 0$
5. $A \cdot (B + C) = A \cdot B + A \cdot C$	6. $A + 0 = A$
7. $A + 1 = 1$	8. $A \cdot 1 = A$
9. $A \cdot 0 = 0$	10. $A \cdot B = B \cdot A$
11. $A + B = B + A$	12. $B \cdot (A + \bar{A}) = B$
13. $A + A \cdot B = A$	14. $A \cdot (A + B) = A$
15. $A + \bar{A} \cdot B = A + B$	16. $A \cdot (\bar{A} + B) = A \cdot B$
17. $\overline{A + B} = \bar{A} \cdot \bar{B}$	18. $\overline{A \cdot B} = \bar{A} + \bar{B}$

## De Morgan's Theoram

De Morgan has suggested two theorems which are extremely useful in Boolean Algebra. The two theorems are discussed below.

### Theorem 1

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

NAND = Bubbled OR

- The left hand side (LHS) of this theorem represents a NAND gate with inputs A and B, whereas the right hand side (RHS) of the theorem represents an OR gate with inverted inputs.

- This OR gate is called as **Bubbled OR**.

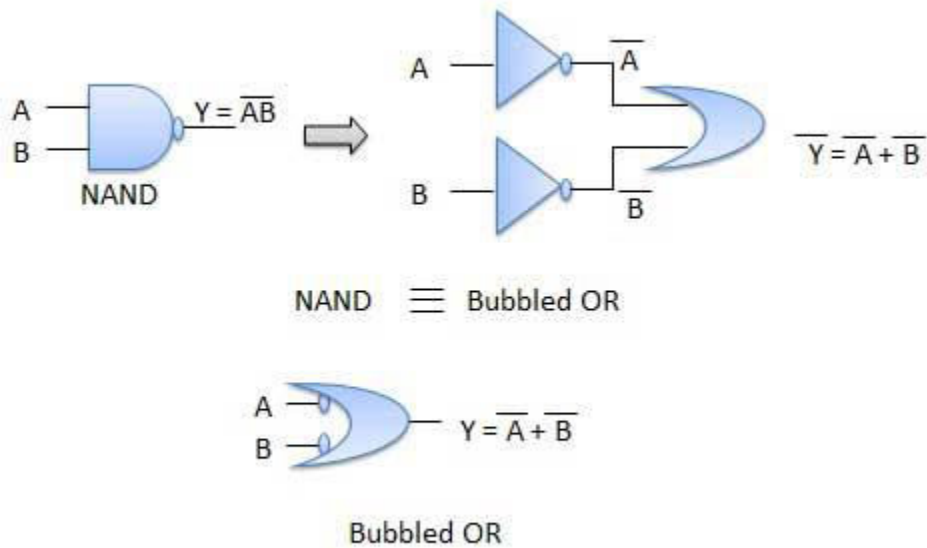


Table showing verification of the De Morgan's first theorem –


A	B	$\overline{AB}$	$\overline{A}$	$\overline{B}$	$\overline{A} + \overline{B}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

## Theorem 2

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

NOR = Bubbled AND

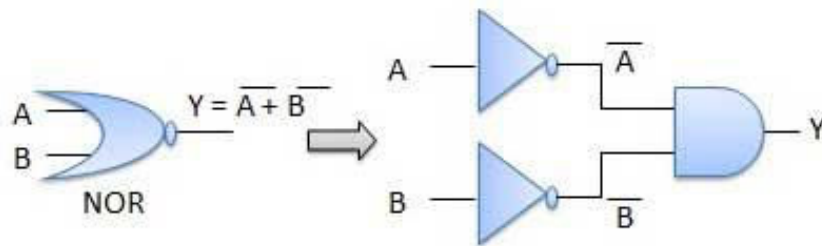- The LHS of this theorem represents a NOR gate with inputs A and B, whereas the RHS represents an AND gate with inverted inputs.
- This AND gate is called as **Bubbled AND**.



NOR  $\equiv$  Bubbled AND

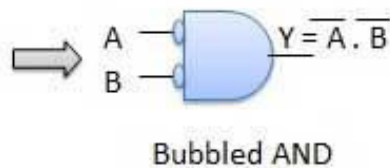


Table showing verification of the De Morgan's second theorem –

A	B	$\overline{A + B}$	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0